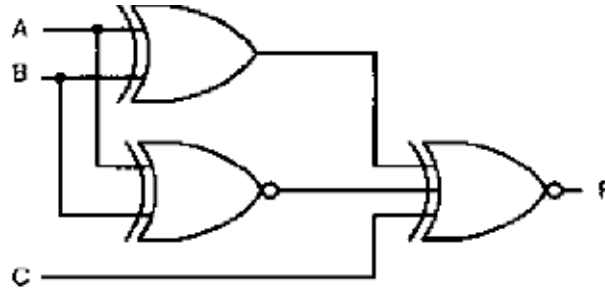


Q.12 For the output F to be 1 in the logic circuit shown, the the input combination should be:



Options:

- | | |
|---------------------------|---------------------------|
| (A) $A = 1, B = 1, C = 0$ | (C) $A = 0, B = 1, C = 0$ |
| (B) $A = 1, B = 0, C = 0$ | (D) $A = 0, B = 0, C = 1$ |

Solution:

- The circuit contains two logic gates receiving inputs A , B , and C . From the diagram:

- The first gate is an OR gate taking inputs A and B : output = $A + B$
- The second gate is a NOR gate taking the same inputs A and B : output = $\overline{A + B}$
- These two outputs are fed into an XOR gate: output = $(A + B) \oplus \overline{A + B}$
- The result of the XOR is then passed into an OR gate with input C : output $F = [(A + B) \oplus \overline{A + B}] + C$

- Now simplify:

$$(A + B) \oplus \overline{A + B} = 1 \quad (\text{since any value XOR its complement is 1})$$

$$F = 1 + C = 1 \quad (\text{since OR with 1 gives 1})$$

- So, for any values of A and B (as long as the circuit logic is valid), the output of the XOR will be 1, and OR-ing it with any C gives $F = 1$. Hence, ****all options result in $F = 1$ ****.
- However, the question asks: “*the input combination should be*” — implying one valid combination is sufficient.
- Option (B): $A = 1, B = 0, C = 0$

$$A + B = 1, \quad \overline{A + B} = 0, \quad \text{XOR} = 1, \quad F = 1 + 0 = 1$$

- So, this is correct.

Correct answer: (B) $A = 1, B = 0, C = 0$