

Abstract

Simulation of latch behavior using Raspberry Pi Pico to demonstrate NAND and NOR latch transitions for the input combinations $(0,1) \rightarrow (1,1)$.

- GP16: NAND Q Output (LED)
- GP17: NOR Q Output (LED)
- GND and VBUS properly connected

1. Components

2. Setup

- GP15: Input P1 (Push Button)
- GP14: Input P2 (Push Button)

3. Observation

- **NAND Latch:** $(0,1) \rightarrow (1,0) \rightarrow$ holds at $(1,0)$
- **NOR Latch:** $(0,1) \rightarrow (1,0) \rightarrow$ transitions to $(0,0)$

4. Truth Tables


NAND Latch

$P1$	$P2$	Output ($Q1, Q2$)
0	1	$(1, 0)$
1	1	$(1, 0)$ (holds)

NOR Latch

$P1$	$P2$	Output ($Q1, Q2$)
0	1	$(1, 0)$
1	1	$(0, 0)$

5. Circuit Image

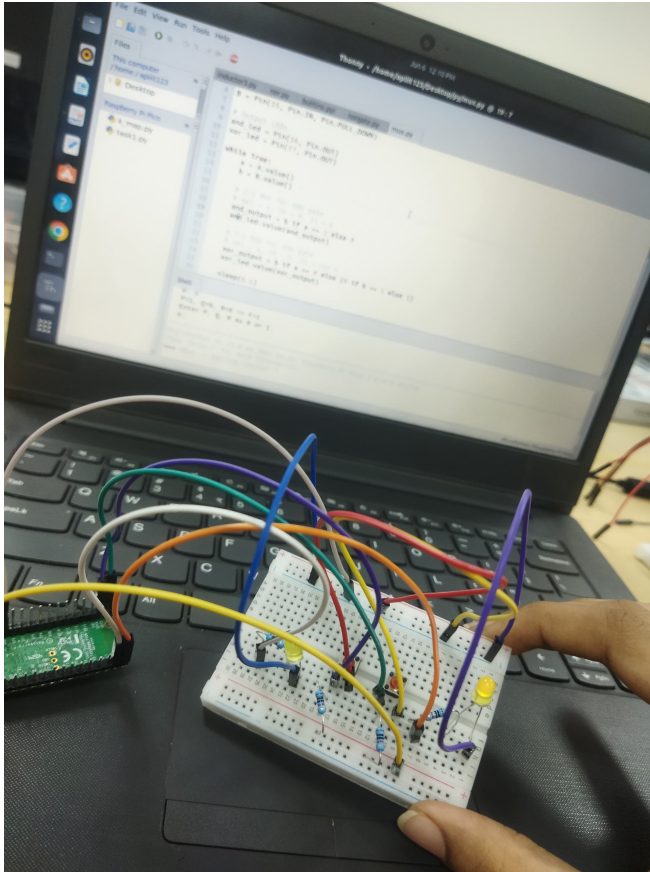

6. GitHub Code Link

<https://github.com/sathvi2710/fwc/blob/main/hardware/platformio/plaformio.py>

7. Conclusion

This project successfully demonstrates latch behavior for NAND and NOR gates using MicroPython and Raspberry Pi Pico.